

Sheet 1

20) $N_1 = 50, N_2 = 10, V_1 = 440V, f = 50Hz, S = 10kVA$

a) $V_2 = V_1 \frac{N_2}{N_1} = 440 \times \frac{10}{50} = 88V$

b) $S = V_1 I_1 = V_2 I_2$

$\therefore I_1 = \frac{S}{V_1} = \frac{10k}{440} = 22,72A$

$I_2 = \frac{S}{V_2} = \frac{10k}{88} = 113,63A$

c) $\phi_m = \frac{E_1}{4.44 N_1 f} = \frac{440}{4.44 \times 50 \times 50} = 0.0396 \text{ Wb}$

21) $N_1 = 350, N_2 = 1050, V_1 = 400V, f = 50Hz, A = 50cm^2$

i) $B_{max} = \frac{E_1}{4.44 N_1 f A} = \frac{400}{4.44 \times 350 \times 50 \times 50 \times 10^{-4}} = 1.03 \text{ Wb/m}^2$

22) $I_\phi = 10A, P_F = 0.25$, $V_1 = 400V, f = 50Hz$

a) $\theta = \cos^{-1}(0.25) = -75,52$

$I_c = I_\phi \cos \theta = 2,5A$

$I_m = I_\phi \sin \theta = 9,68A$

* b)

c) $N_1 = 500 \rightarrow \phi_{max} = \frac{V_1}{4.44 N_1 f} = \frac{400}{4.44 \times 500 \times 50} = 3,6 \times 10^{-3}$

23) $S = 15 \text{ kVA}$, $V_1 : V_2 = 2200 : 110 \text{ V}$, $R_1 = 4.75 \Omega$, $R_2 = 0.0045 \Omega$
 $X_1 = 2.6 \Omega$, $X_2 = 0.0075 \Omega$

a) $R_{eq1} = R_1 + \bar{R}_2 = R_1 + a^2 R_2 = 4.75 + \left(\frac{2200}{110}\right)^2 \cdot 0.0045$
 $= 6.55 \Omega$

b) $R_{eq2} = \bar{R}_1 + R_2 = \frac{R_1}{a^2} + R_2 = 4.75 \left(\frac{110}{2200}\right)^2 + 0.0045$
 $= 0.0163 \Omega$

c) $X_{eq1} = X_1 + \bar{X}_2 = X_1 + a^2 X_2 = 2.6 + \left(\frac{2200}{110}\right)^2 \cdot 0.0075$
 $= 5.6 \Omega$

d) $X_{eq2} = \bar{X}_1 + X_2 = \frac{X_1}{a^2} + X_2 = \frac{2.6}{\left(\frac{2200}{110}\right)^2} + 0.0075$
 $= 0.014 \Omega$

e) $Z_{eq1} = R_{eq1} + j X_{eq1} = 6.55 + j 5.6$

f) $Z_{eq2} = R_{eq2} + j X_{eq2} = 0.0163 + j 0.014$

* g)

* 24) $V_1 : V_2 = 250 : 225$, $S = 5 \text{ kVA}$, $R_1 = 0.2 \Omega$, $X_1 = 0.75 \Omega$
 $R_2 = 0.05 \Omega$, $X_2 = 0.2 \Omega$.

25) $S = 5 \text{ kVA}$, $V_1: V_2 = 500:250$, $f = 50 \text{ Hz}$

O.C (L.V open) \rightarrow ref to High

S.C (L.V short) \rightarrow ref to High

	V	I	P
O.C	500	1	50
S.C	25	10	60

$$a) \eta = \frac{n (V.A)_{f_1} \cos \theta}{n (V.A)_{f_1} \cos \theta + P_o + n^2 (P_{cu})_{f_1}} * 100 \quad \left. \begin{array}{l} P.F = 0.8 \\ \text{lag} \end{array} \right\}$$

$$n = \frac{100}{100} \text{ full load } (V.A)_{f_1} = S = 5 \text{ kVA}$$

$$P_o = P_{o.c} = 50 \text{ W}, \quad P_{cu} = P_{s.c} = 60 \text{ W}$$

$$\eta = \frac{5000 * 0.8}{5000 * 0.8 + 50 + 60} * 100 = 97.3 \%$$

$$b) V.R = \frac{V_s (\text{no Load}) - V_s (\text{full load})}{V_s (\text{full load})} * 100$$

$$V_s (FL) = V_2 = 250 \text{ V}$$

$$V_s (\text{no load}) = V_p$$

$$V_p = I_s Z_{eq} + V_s$$

$$I_s = I_{s.c} \angle \cos^{-1}(0.8) = 10 \angle -36.86$$

$$Z_{eq} (\text{From Short Circuit test in (d)}) =$$

$$\text{then } V_p = 10 \angle -36.86 * 2.5 + 250 = 270 \angle -3.17$$

$$\text{then } V.R = \frac{270 - 250}{250} * 100 = 8 \%$$

c) From (a) then, at 60% full


$$\eta = \frac{\frac{60}{100} \times 5000 \times 0.8}{\frac{60}{100} \times 5000 \times 0.8 + 50 + \left(\frac{60}{100}\right)^2 \times 60} \times 100 = 97.1\%$$

d) * First O.C test

$$P_{o.c} = V_{o.c} I_{o.c} \cos \theta$$

$$\therefore \theta = \cos^{-1} \left(\frac{P_{o.c}}{V_{o.c} I_{o.c}} \right) = \left(\frac{50}{500 \times 1} \right) V_1$$

$$= 84.26$$

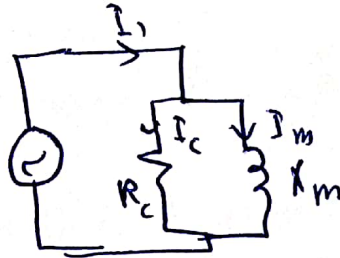

$$I_c = I_{o.c} \cos \theta = 1 \cos (84.26) = 0.1 A$$

$$I_m = I_{o.c} \sin \theta = 0.994 A$$

$$R_c = \frac{V_{o.c}}{I_c} = 5000 \Omega, X_m = \frac{V_{o.c}}{I_m} = 503 \Omega \left\{ \begin{array}{l} \text{Ref to} \\ \text{High} \\ \text{(Primary)} \end{array} \right.$$

* Second S.C test

$$\theta = \cos^{-1} \left(\frac{P_{s.c}}{V_{s.c} I_{s.c}} \right) = \left(\frac{60}{25 \times 10} \right) V_1$$


$$= 76.1$$



$$Z_{eq} = \frac{V_{s.c}}{I_{s.c}} = \frac{25}{10} = 2.5 \Omega$$

$$R_{eq} = Z_{eq} \cos \theta = 0.6 \Omega, X_{eq} = Z_{eq} \sin \theta = 2.426 \Omega \left\{ \begin{array}{l} \text{Ref} \\ \text{to H} \end{array} \right.$$

* Circuit Ref to Primary

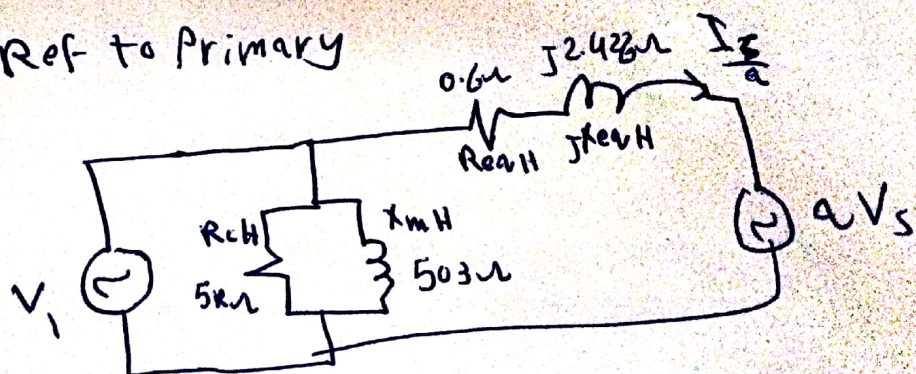

26)

نفس الفكرة ومديلا ار Zea جامعة

27), 28)

نفس فكرة ٢٩ إلى

منحليها الآن بس فيها زيادة

29)

$$S = 10 \text{ KVA}, V_1 : V_2 = 220 : 110$$

$$R_1 = 0.02 \Omega, R_2 = 0.01 \Omega, R_c = 2000 \Omega$$

$$X_1 = 0.04 \Omega, X_2 = 0.01 \Omega, X_m = 3000 \Omega$$

75% of Full load, Unity Power (P.F = 1)

a) referred to Primary (APPROXIMATE)

$$a = \frac{N_1}{N_2} = \frac{V_1}{V_2} = 2$$

$$\bar{V}_2 = a V_2 = 220$$

$$R_{eq1} = R_1 + R_2' = R_1 + a^2 R_2 = 0.02 + 4 \times 0.01 = 0.06 \Omega$$

$$X_{eq1} = X_1 + X_2' = X_1 + a^2 X_2 = 0.04 + 4 \times 0.01 = 0.08 \Omega$$

$$I_{2(FU)} = \frac{S}{V_2} = \frac{10 \text{ K}}{110} = 90.91 \text{ A}$$

$$\bar{I}_{2(FU)} = \frac{I_{2(FU)}}{a} = 45.45 \text{ A}$$

$$\bar{I}_2 = \frac{75}{100} \bar{I}_{2(FU)} = 34.1 \text{ A} \quad \text{or } \bar{I}_2 = \frac{75}{100} * \frac{S}{V_2} = 34.1 \text{ A}$$

$$\theta = \cos^{-1}(1) = 0 \rightarrow I_2' = 34.1 \angle 0^\circ \text{ A}$$

$$V_1 = E = I_2' (R_{eq1} + jX_{eq1}) + V_2' = 222.06 \angle 0.703^\circ \text{ V}$$

$$I_1 = I_\phi + I_2' = I_c + I_m + I_2' = \frac{E}{R_c} + \frac{E}{jX_m} + I_2'$$

$$\therefore I_1 = 35.23 \angle -1.18^\circ \text{ A}$$

* b)

$$c) \eta = \frac{V_2 I_2' \cos(\theta_{V_2} - \theta_{V_1})}{V_1 I_1 \cos(\theta_{V_1} - \theta_{I_1})} = \frac{V_2 I_2' \cos \theta_2}{V_1 I_1 \cos \theta_1} * 100 = \frac{220 * 34.1 \cos(0 - 0)}{222.06 * 35.23 \cos(0.741 - 1.18)} * 100 \approx 96 \%$$

30) Like (25)

25) ref to secondary

$$\therefore R_{CH} = 5000, \quad X_{MH} = 503$$

$$R_{eqH} = 0.6, \quad X_{eqH} = 2.43$$

then

$$R_{CL} = \frac{R_{CH}}{a^2} = 5000 \div \left(\frac{500}{250}\right)^2 = 1250\Omega$$

Same with

$$X_{ML} = 125.75$$

$$R_{eqL} = 0.15$$

$$X_{eqL} = 0.607$$


*when LV open or short then it is reference to Primary

When HV open or short then it is reference to Secondary

if ~~test~~ short test in H.V then it is ref to High


Same if test in L.V then it is ref to Low

Circuit ref to secondary

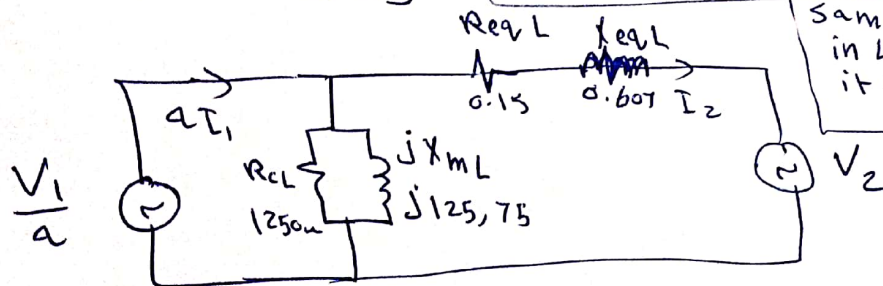

*ideal Tr. circuit

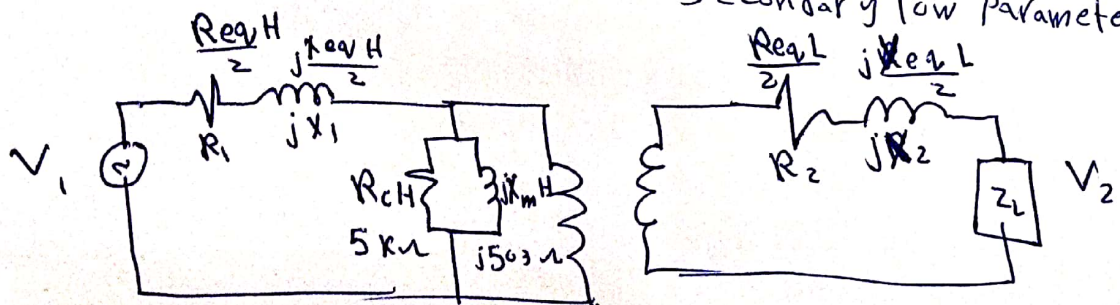(Primary high Parameters
Secondary low Parameters)



$$R_1 = \frac{R_{eqH}}{2} = \frac{0.6}{2} = 0.3\Omega, \quad \text{Same } X_1 = \frac{2.43}{2} = 1.215\Omega$$

$$R_2 = \frac{R_{eqL}}{2} = \frac{0.15}{2} = 0.075\Omega, \quad \text{Same } X_2 = \frac{0.607}{2} = 0.3\Omega$$

$$\text{assume } R_1 = R_2, \quad X_1 = X_2$$